

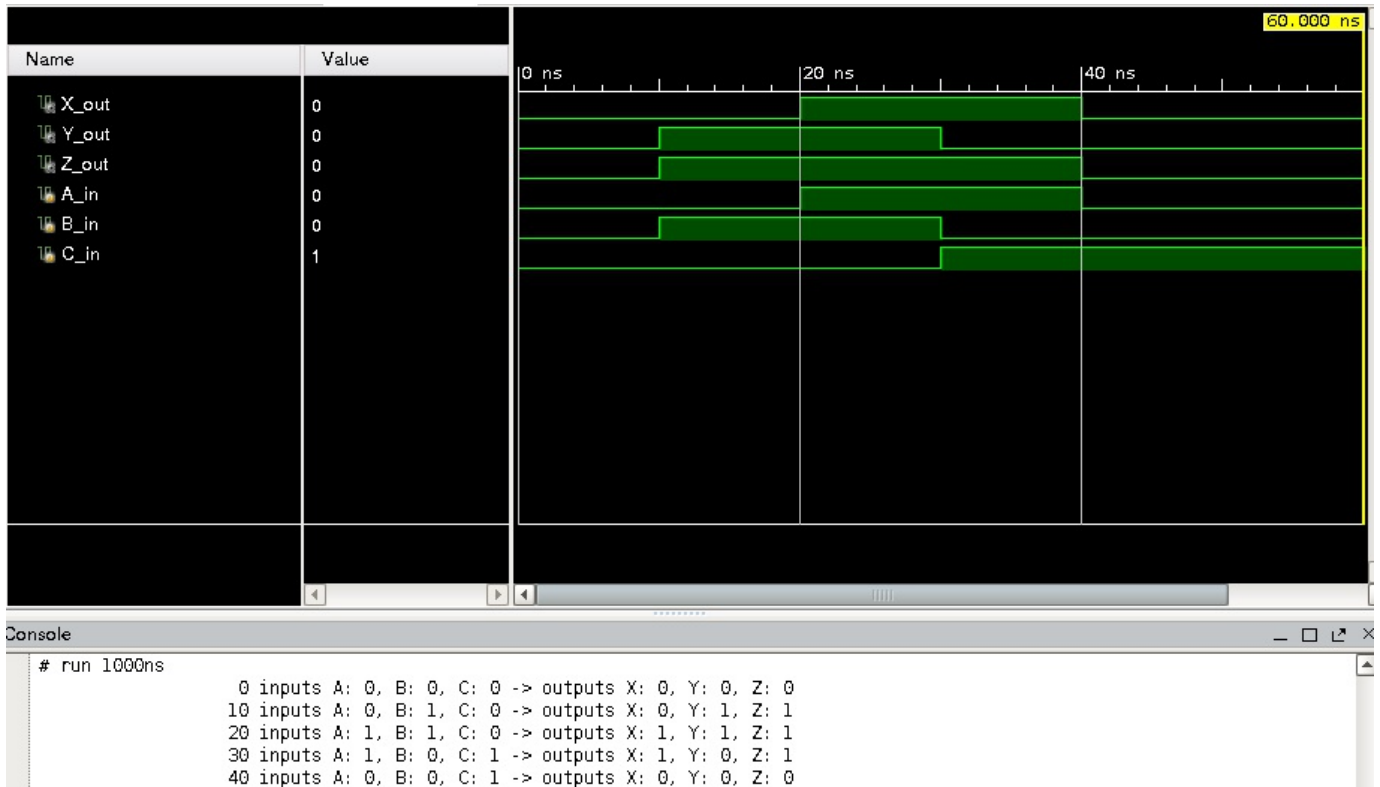



1.

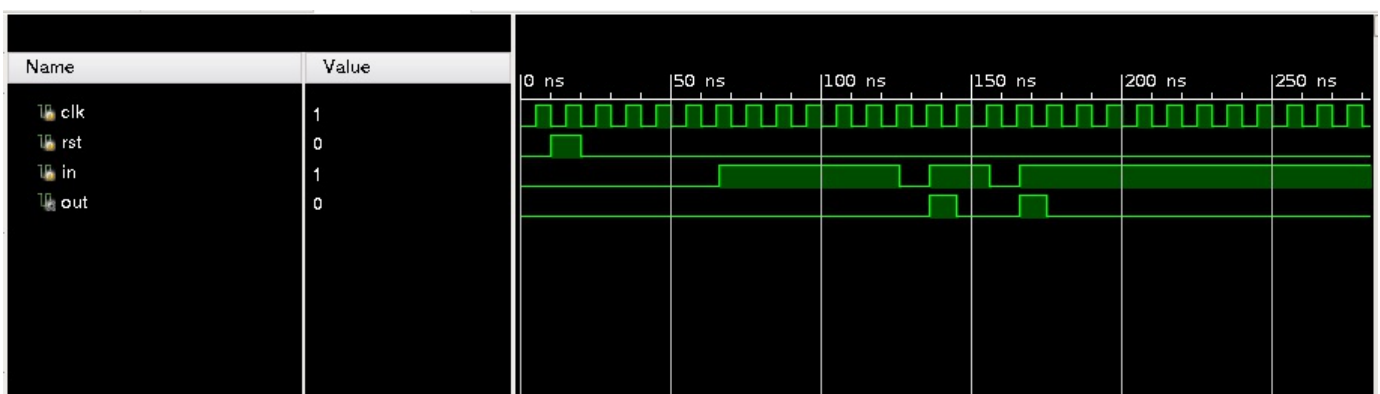

waveform of three different implementation are exactly the same, here I only attached one, others were include in the folder

2.

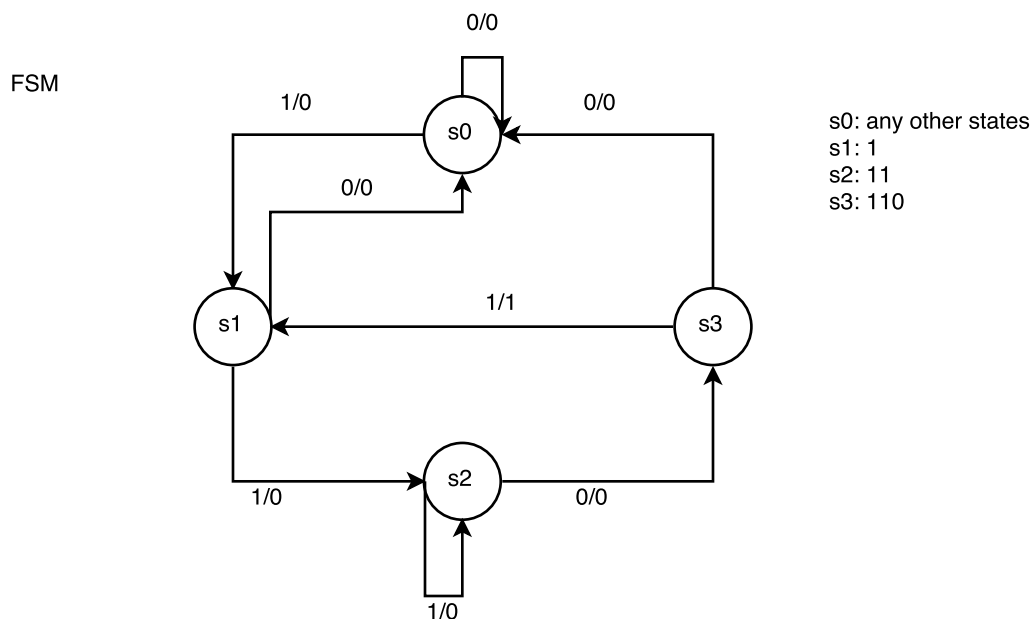

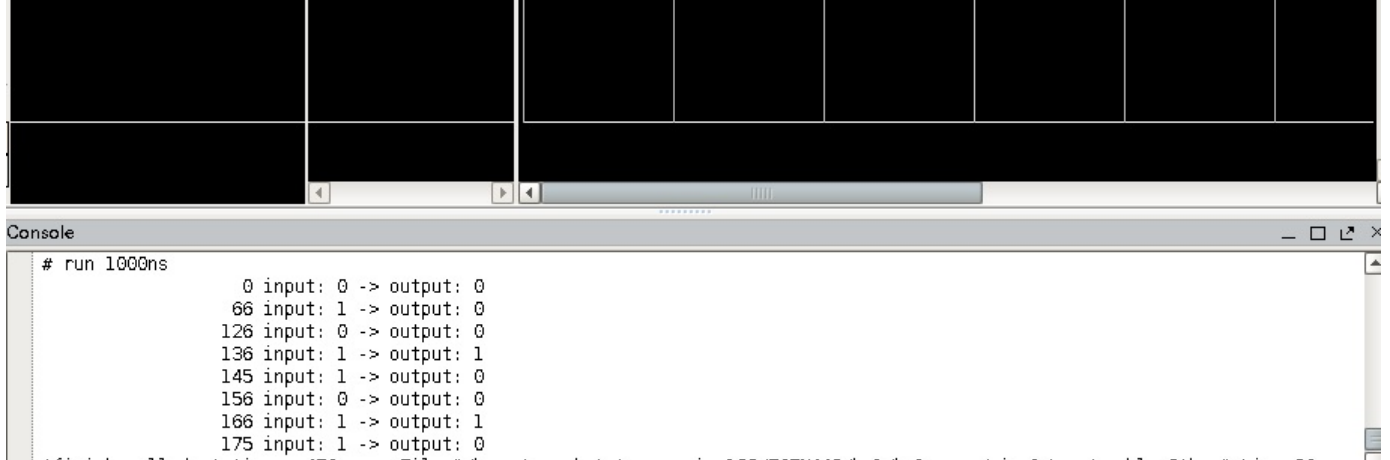


- in the 4-bit ripple adder, at time 100, the two inputs change to 0001, the carry in is 1
the correct output was produced at time 103


in the 8-bit ripple adder, at time 100, the two inputs change to 11110001 and 01010001, the carry in is 1
the correct output was produced at time 105

the delay was produced when the output of XOR / AND / OR gate changed, the delay time is depend on inputs and carry in.

4-bit ripple adder

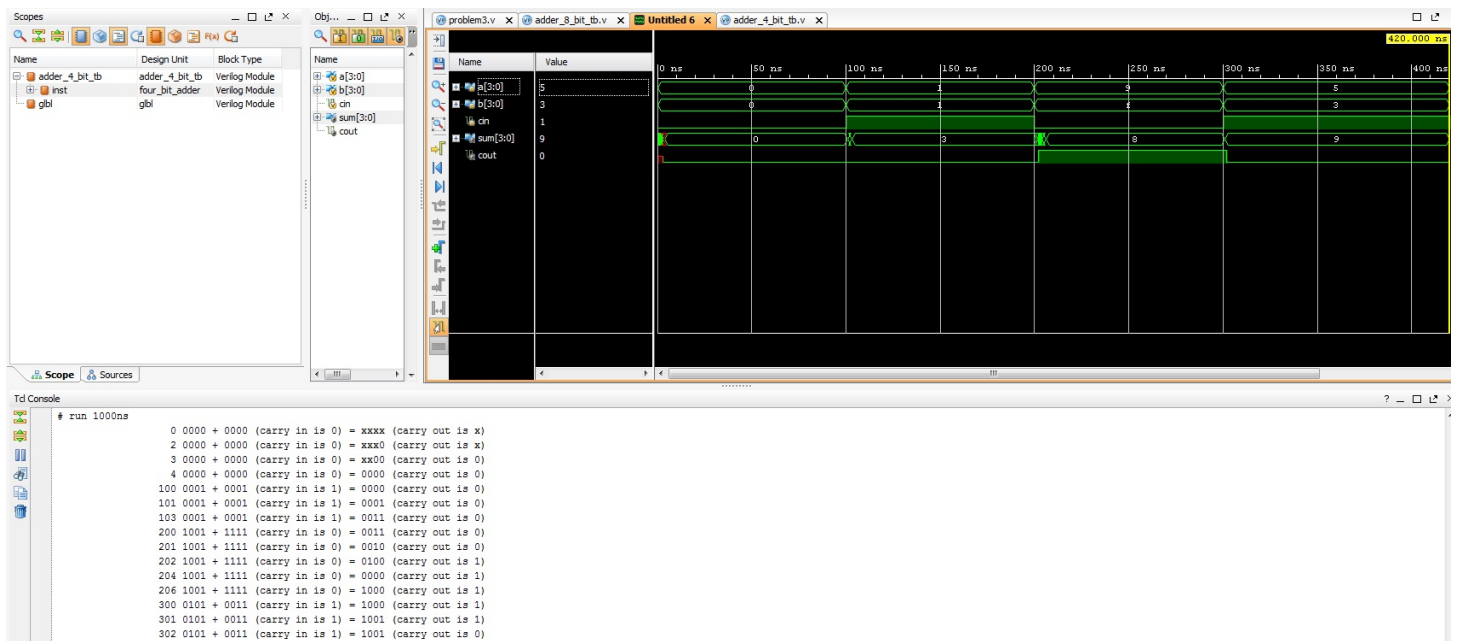

8-bit ripple adder

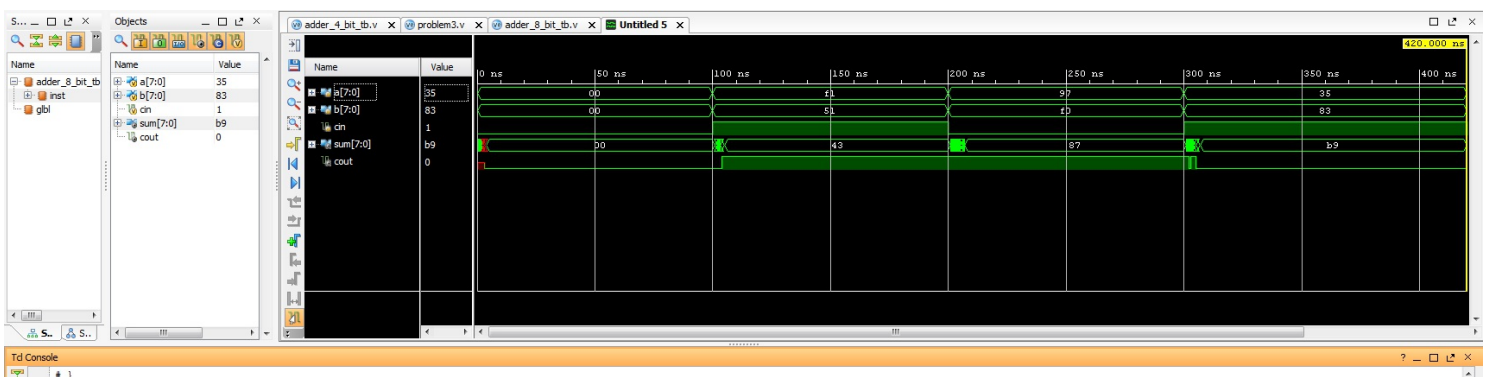


```

# run 1000ns
0 00000000 + 00000000 (carry in is 0) = xxxxxxxx (carry out is x)
2 00000000 + 00000000 (carry in is 0) = xxxxxxx0 (carry out is x)
3 00000000 + 00000000 (carry in is 0) = xxxxxxx0 (carry out is 0)
4 00000000 + 00000000 (carry in is 0) = 00000000 (carry out is 0)
100 11110001 + 01010001 (carry in is 1) = 00000000 (carry out is 0)
101 11110001 + 01010001 (carry in is 1) = 00000001 (carry out is 0)
102 11110001 + 01010001 (carry in is 1) = 10100001 (carry out is 0)
103 11110001 + 01010001 (carry in is 1) = 00000011 (carry out is 0)
104 11110001 + 01010001 (carry in is 1) = 00000011 (carry out is 1)
105 11110001 + 01010001 (carry in is 1) = 01000011 (carry out is 1)
200 10010111 + 11110000 (carry in is 0) = 01000011 (carry out is 1)
201 10010111 + 11110000 (carry in is 0) = 01000010 (carry out is 1)
202 10010111 + 11110000 (carry in is 0) = 10000101 (carry out is 1)
203 10010111 + 11110000 (carry in is 0) = 00000111 (carry out is 1)
204 10010111 + 11110000 (carry in is 0) = 10000011 (carry out is 1)
205 10010111 + 11110000 (carry in is 0) = 10000111 (carry out is 1)
206 10010111 + 11110000 (carry in is 0) = 10001111 (carry out is 1)
207 10010111 + 11110000 (carry in is 0) = 10000111 (carry out is 1)
300 00110101 + 10000011 (carry in is 1) = 10000111 (carry out is 1)
301 00110101 + 10000011 (carry in is 1) = 10000110 (carry out is 1)
302 00110101 + 10000011 (carry in is 1) = 01010111 (carry out is 0)
303 00110101 + 10000011 (carry in is 1) = 01110101 (carry out is 1)
304 00110101 + 10000011 (carry in is 1) = 11110101 (carry out is 1)
305 00110101 + 10000011 (carry in is 1) = 10110001 (carry out is 0)

```

4.

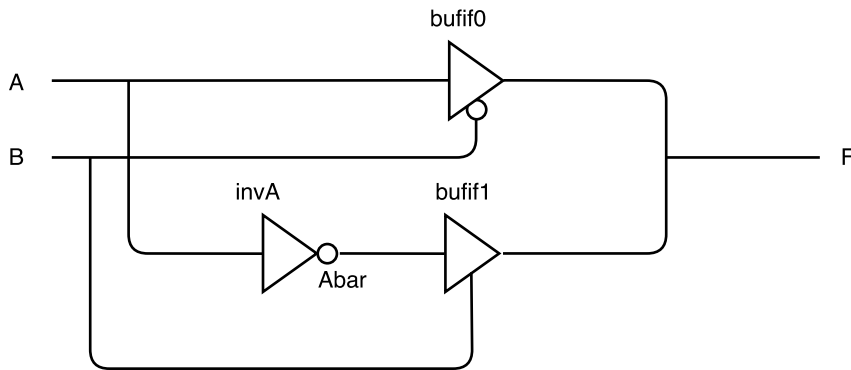

The functionality of my design is to control outputting the input value or its reverse.

